

# AN12342

## Card Coil Design Guide for MIFARE DESFire Light

Rev. 1.0 — 31 January 2019

522610

Application note  
COMPANY PUBLIC

### Document information

Information	Content
Keywords	Contactless, MIFARE DESFire Light, ISO/IEC 14443, Resonance, Coil, Inlay, Antenna
Abstract	This document provides guidance for engineers designing magnetic loop antenna coils for MIFARE DESFire Light ICs



Revision history		
Rev	Date	Description
1.0	20190131	Initial version

## 1 Introduction

MIFARE DESFire Light, a passive device (without battery) is powered by a magnetic field generated by the PCD. To get the magnetic flux cut by the PICC, it requires also a loop antenna.

This document describes some notes to the design of loop antennas for MIFARE DESFire Light. The detailed loop antenna design is explained in [1]. Although such antennas are relatively straightforward in principle and look very similar when comparing various contactless smartcards, experience proves that their parameters do have a noticeable impact on performance.

In this document, some antenna layout examples are attached for your reference but please adapt and verify them before you go for production. In this document the term „MIFARE DESFire Light card“ refers to a MIFARE DESFire Light IC-based contactless card.

### 1.1 How to use this document

In this document only the antenna design hints and notes specific to MIFARE DESFire Light are explained. All the basics and design details are explained in [1]. Please use [1] as the base document and apply wherever requires the notes mentioned here.

### 1.2 Terms and Abbreviations

Table 1. Abbreviations

Acronym	Description
CCDG	Card Coil Design Guide
PCD	Proximity Coupling Device
PICC	Proximity IC Card

## 2 Card Coil Design Notes for MIFARE DESFire Light

There are different classes of antennas widely used in contactless applications for the MIFARE DESFire Light PICC. For different antenna classes the design of PICC coils are different. Even different application requirements also lead to different antenna design.

Basically, three parameters are important for the card coil design: coil area, coil quality factor and resonance frequency of the transponder under loaded conditions.

### 2.1 Different classes of antenna according to ISO/IEC 14443-1

In [Figure 1](#) different antenna sizes according to ISO/IEC 14443-1 [4] are shown.

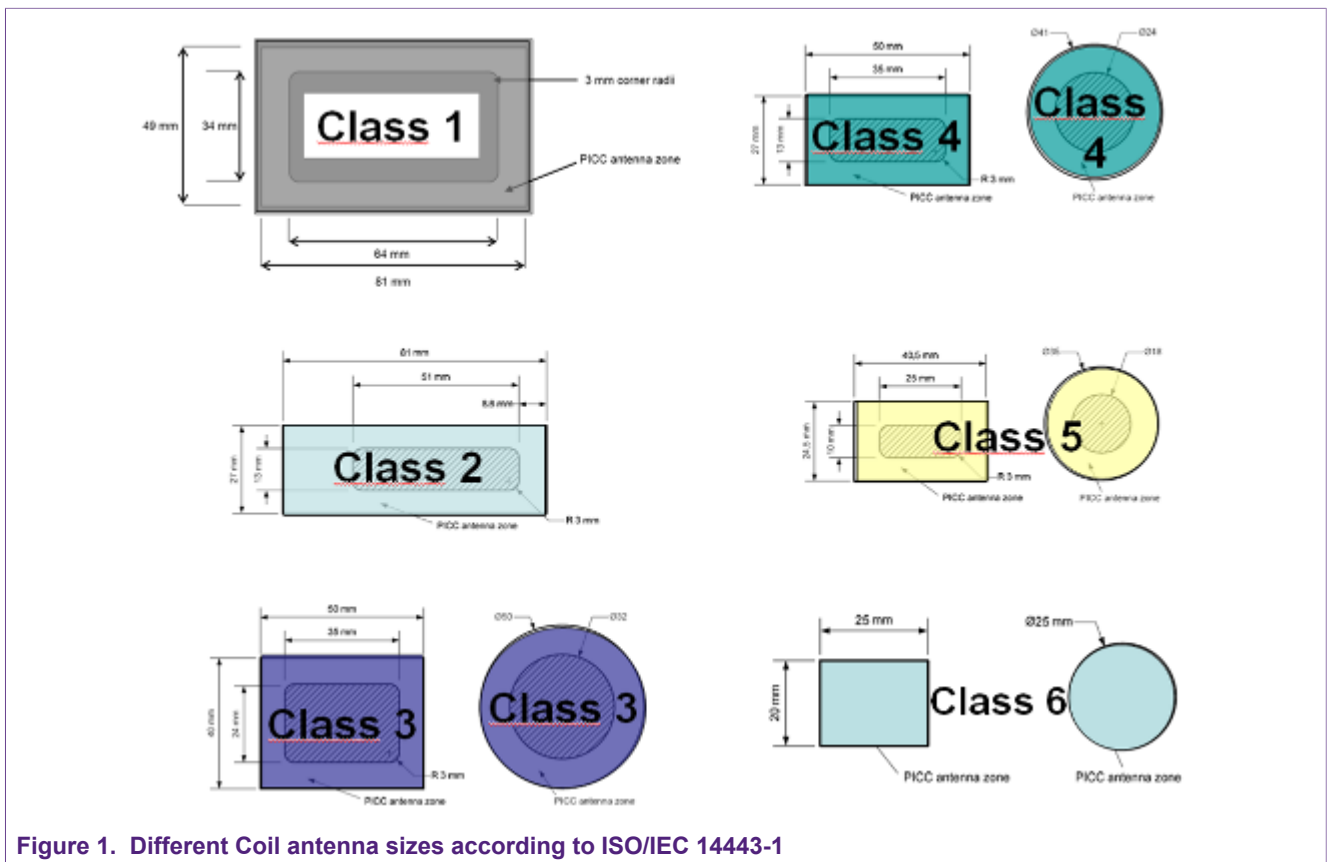


Figure 1. Different Coil antenna sizes according to ISO/IEC 14443-1

### 2.2 Average card coil area

Make the card coil area as big as possible. Rounded corners are better than sharp corners.

### 2.3 Coil Q-Factor

To achieve best performance and to cover manufacturing tolerances, for MIFARE DESFire Light, the recommended Coil Q values are given in [Table 2](#).

### 2.3.1 Measurement of Coil Q-Factor

There are different ways to measure the Q-Factor of the coil antenna, which may end up with different results. Follow the way described in the Card Coil Design Guide [\[1\]](#) or ask your NXP technical support.

## 2.4 Definition for “unloaded” and “loaded” conditions.

“**loaded conditions**”, or just “loaded”, means that the MIFARE DESFire Light IC gets enough power to be able to fully operate. With the NXP setup used (defined in [\[2\]](#)), those conditions are achieved, when the power at the network analyzer output is set to the value of +10 dBm.

“**unloaded conditions**”, or just “unloaded”, means that the MIFARE DESFire Light IC doesn't get enough power in order to even start to operate. With the NXP setup used (defined in [\[2\]](#)), those conditions are achieved, when the power at the network analyzer output is set to the value of -30 dBm.

Both conditions were created with a NXP dedicated measurement setup, which is described in [\[2\]](#). All measurement results presented further down in this document have been obtained with this setup and under “loaded” and “unloaded” conditions as defined earlier in this paragraph.

## 2.5 Loaded resonance frequency of the transponder

The loaded resonance frequency of the transponder is the resulting resonance frequency, if the MIFARE DESFire Light contactless IC is operated under loaded conditions.

In general, the appropriate resonance frequency of the transponder depends on the input capacitance of the MIFARE DESFire Light IC. To achieve best performance and to cover manufacturing tolerances, for MIFARE DESFire Light, the recommend loaded resonance frequency is given in [Table 2](#).

### 2.5.1 Measurement of loaded resonance frequency of the transponder

There are different ways to measure the resonance frequency of the transponder, which may end up with different results. Follow the way described in the Card Coil Design Guide [\[1\]](#) or ask your NXP technical support.

## 2.6 NXP recommendation for PICC coil design

[Table 2](#) summarizes the recommendations for PICC coil design.

Table 2. PICC coil design recommendation

Antenna class	Recommended chip of MIFARE DESFire Light	Recommended loaded transponder resonance frequency ( $f_R$ )	Recommended Coil Q	Comments
Class 1	17 pF	13.56 MHz < $f_R$ < 16 MHz	> 30	Transponder optimum loaded resonance frequency for single card operation is close to 14.5MHz. Transponder optimum loaded resonance frequency for stacked 2 cards operation is close to 15.5MHz.
Class 2	50 pF	13.56 MHz < $f_R$ < 14.50 MHz	> 40	For 106 kbps and single card application. The optimum loaded resonance frequency is slightly above 13.56 MHz.
Class 3	50 pF	13.56 MHz < $f_R$ < 14.50 MHz	> 40	For 106 kbps and single card application. The optimum loaded resonance frequency is slightly above 13.56 MHz.
Class 4	50 pF	13.56 MHz < $f_R$ < 14.50 MHz	> 40	For 106 kbps and single card application. The optimum loaded resonance frequency is slightly above 13.56 MHz.
Class 5	50 pF	13.56 MHz < $f_R$ < 14.50 MHz	> 40	For 106 kbps and single card application. The optimum loaded resonance frequency is slightly above 13.56 MHz.
Class 6	50 pF	13.56 MHz < $f_R$ < 14.10 MHz	> 40	For 106 kbps and single card application. The optimum loaded resonance frequency is slightly above 13.56 MHz.

Those recommended quality factor values for the coil are important to get the best power transfer and to increase the so-called power range of the transponder. Those recommended values will also remain valid for higher bit rates than 106 kbps (up to 848 kbps).

For Class 1 antennas (17 pF input capacitance IC version) a minimum coil Q-Factor of 30 is recommended. The resulting transponder Q-factor under “unloaded” conditions is similar to this value. Once the IC starts to operate, the transponder (loaded) Q-Factor is decreasing and this is leading to a loaded Q-Factor in the range of Q = 8-9. This value is a good compromise in the middle of the Range Q = 6-15, which results in a good performance for all data transfer rates (from 106 kbps to 848 kbps).

All those considerations are valid as well for class 2 to class 6 antennas (50 pF input capacitance IC version), only difference is that a minimum coil Q-Factor of 40 is recommended.

**Note:** Increasing the communication bit rate may reduce the communication distance especially for the small antennas (smaller than Class 1). This could be caused by insufficient coupling between reader and card antenna, as bigger designed antennas typically show a slight performance margin, but smaller once rather not.


## 2.7 Practical design hints and recommendations for 17 pF chip version

### 2.7.1 Class 1 wire wound antennas

Hints for antenna design:

Within the borders of the application and the card manufacturing processes used, try to maximize the antenna size. The outermost turn of the antenna coil should be placed as close as possible to the edge of the card represented by an 81 x 49 mm rectangle. Class 1 antenna examples (with two different parameters) are shown in [Figure 2](#).

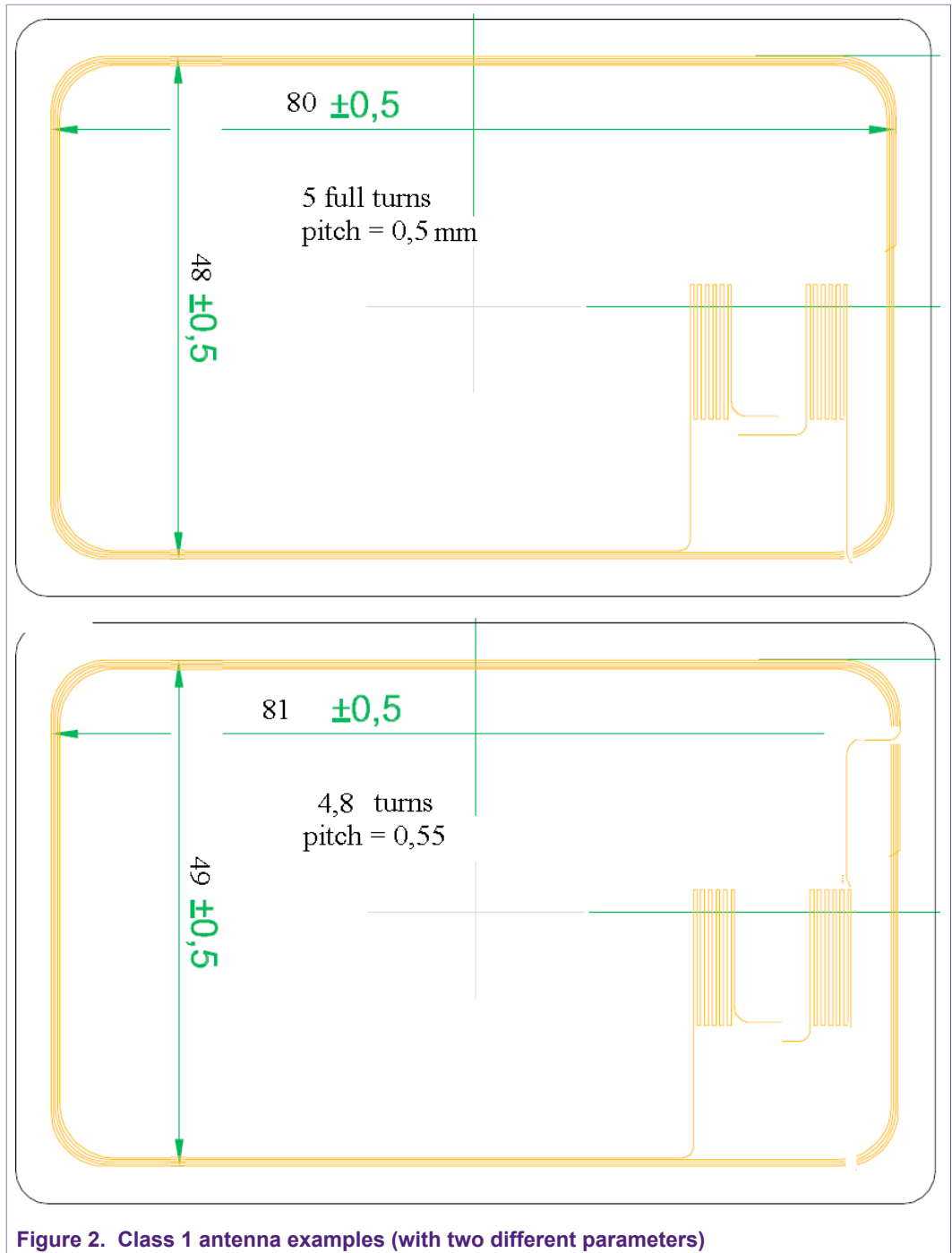**Note:** international standards and industry specifications may restrict the choice of the maximum allowed antenna coil size.



For Class 1 (ID-11 size) antenna, the 17 pF input capacitance IC version is recommended. For all other classes (from ID-2 to ID-6) the usage of the 50 pF input capacitance IC version of the MIFARE DESFire Light chip is recommended.

Figure 3 shows further examples of typical parameters for different ID1-sized antenna designs. Besides geometrical coil parameters (orange colored area), also measured (blue colored area) and calculated (green colored area) electrical parameters are listed in comparison.



Embedded Wire rectangular Antennas								
Dimensions	outline	mm	72.6 x 42	80.2 x 48	80 x 47.5	80 x 48	80.5 x 48	
	wire diam.	mm	0.112	0.112	0.112	0.112	0.112 ?	
	wire pitch	mm	0.14	0.45	0.45	0.45	0.3	
	turns		5	5	4.9	5	5	
measured	Ls @ 1MHz	μH	4.83	4.89	4.69	4.90	5.23	
	Rs Q 1 MHz	Ohm	2.05	2.29	2.22	2.24	2.37	
	fres	MHz	36.84	38.45	42.58	39.46	39.19	
	Rp @ fres	kOhm	55.00	69.00	90.00	90.00	55.00	
	Q @ fres		63.00	66.00	72.00	70.00		
Calculated								
	Cp	pF	3.87	3.51	2.98	3.32	3.16	
	Rs	Ohm	3.92	3.78	3.22	3.38	4.49	
	Q		105.03	110.11	124.00	123.70	99.16	

Figure 3. Typical parameters of different realizations of class 1 card antennas

2.7.2 Class 1 etched antennas

One of possible antenna design realizations is shown in Figure 4.

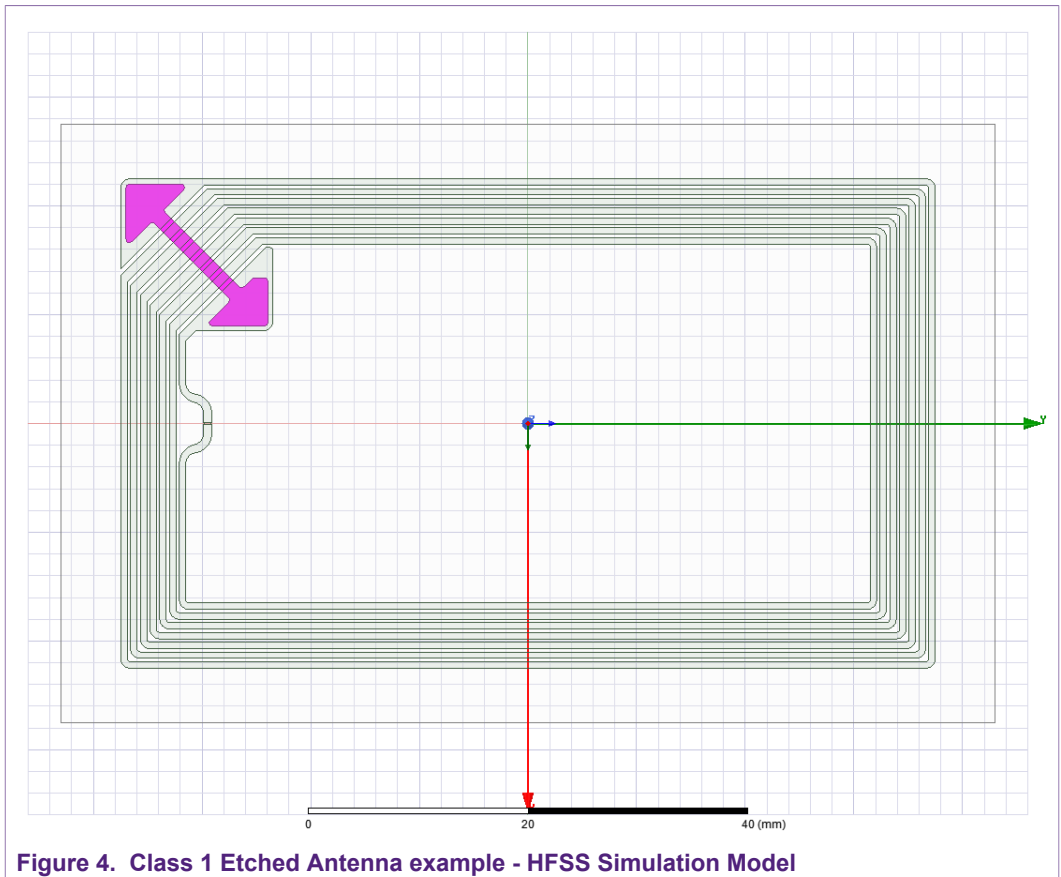


Figure 4. Class 1 Etched Antenna example - HFSS Simulation Model

The geometrical parameters of the antenna are given in Table 3

**Table 3. Geometrical Parameters of a Class 1 etched antenna design**

Parameter	Value
Antenna Dimension, mm x mm	75 x 45
Material:	Aluminum
Trackwidth, mm	0,6
Gap between tracks, mm	0,3
Track thickness (coil), mm	0,03
Track thickness (bridge), mm	0,01
Number of Turns	7
Carrier Material:	Polyester
Carrier Thickness, mm	0,038
Carrier Dielectric constant, Er:	3,2

and simulative electrical parameters are presented in [Table 4](#).

**Table 4. Electrical Parameters of a Class 1 etched antenna design**

Parameter	Value
SRF, MHz	33,6412
R (@1MHz), Ohm	2,3814
L (@1MHz), uH	5,8623
R (@13,56MHz), Ohm	6,8700
L (@13,56MHz), uH	6,9165
C, pF	3,81
Cic, pF	17
Fres_PICC, MHz	14,5200

The drawing of this antenna (in DXF Format) is available and attached to this document.

To verify the simulation results an etched copper prototype has been ([Fig 5](#)) built and evaluated.



Figure 5. Class 1 Etched Antenna example - Prototype

Fig 6 shows a “loaded” resonance frequency and quality factors, whereas Fig 7 shows a “unloaded” resonance frequency and quality factors of the prototype.

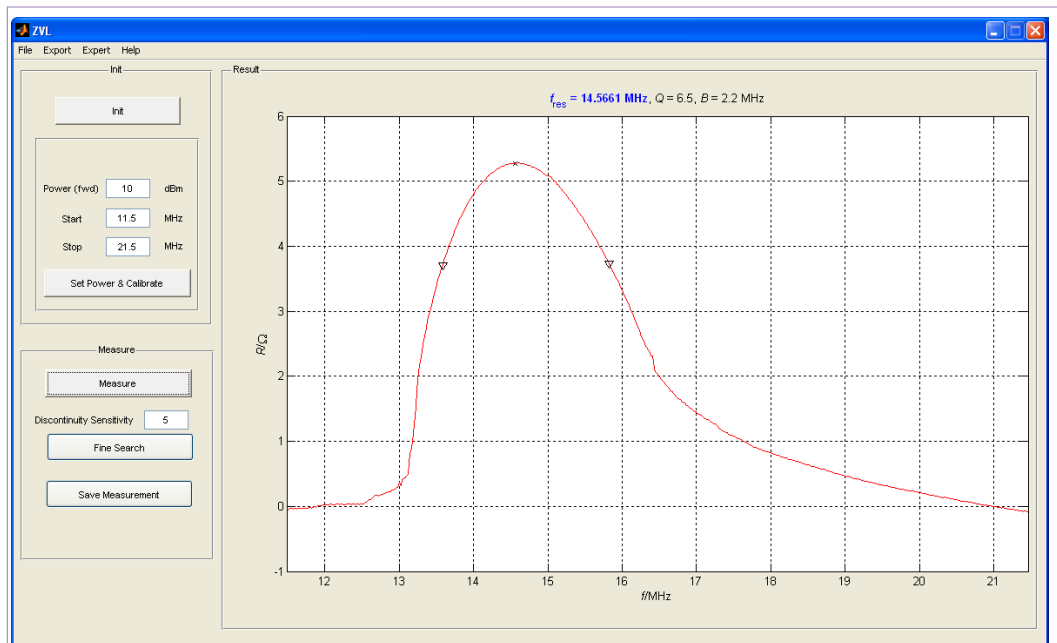


Figure 6. Loaded resonance frequency (14,56 MHz) and Quality factor (6,5) - Prototype

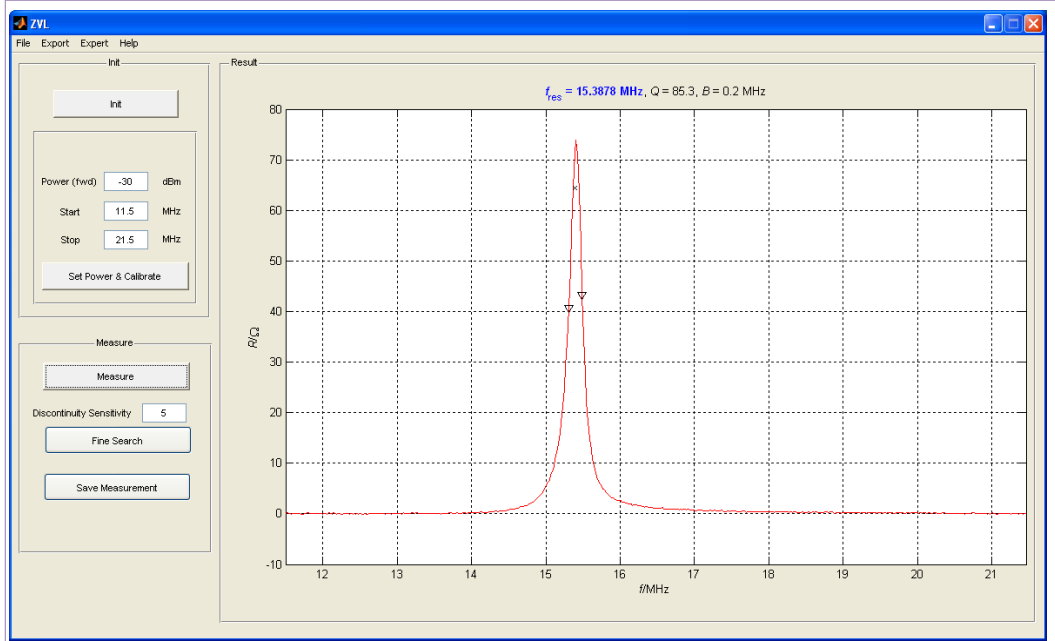


Figure 7. Unloaded resonance frequency (15,39 MHz) and Quality factor (85,3) - Prototype

The label sensitivity (Hmin) at 13,56 MHz is measured to be 0,175 A/m (Fig 8) for Level 3 activation.

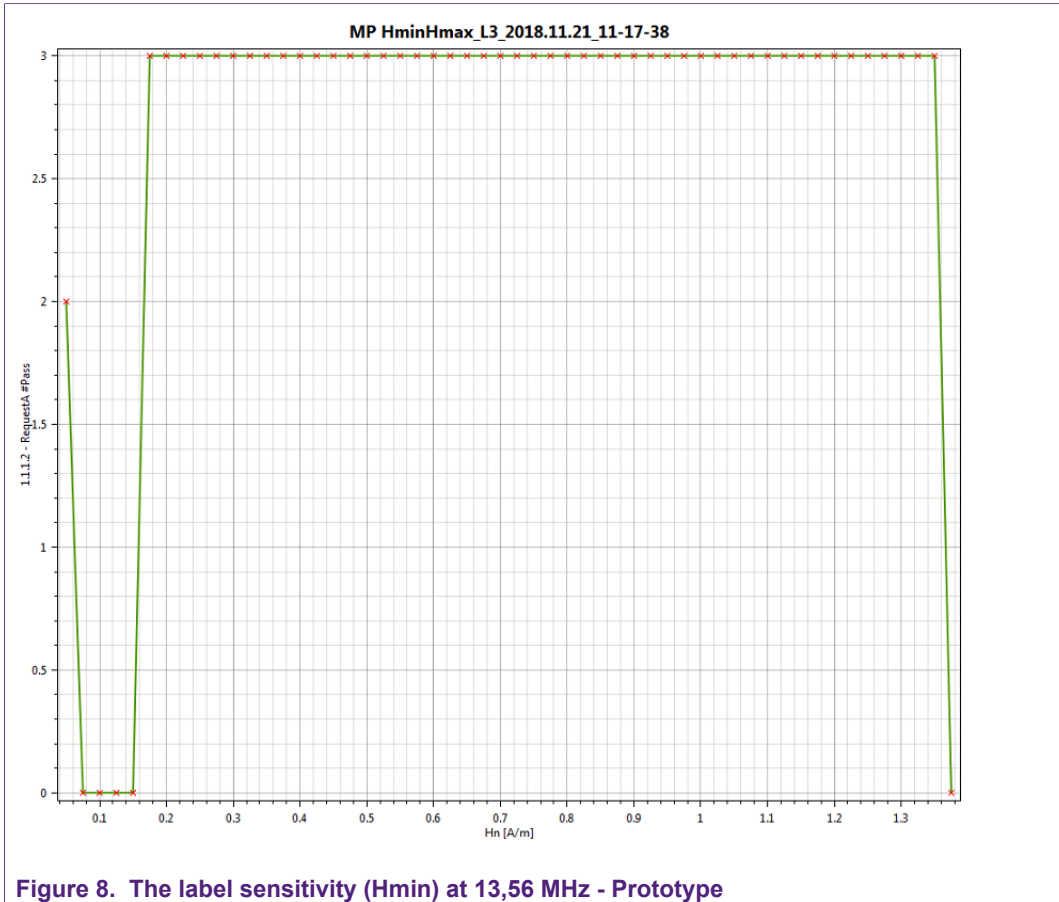



Figure 8. The label sensitivity (Hmin) at 13,56 MHz - Prototype

**2.8 Practical design hints and recommendations for 50 pF chip version**

For Class 2 and up to Class 6 antenna sizes, it is recommended to use 50 pF input capacitance IC version.

**2.8.1 Class 6 etched antenna**

One of possible antenna design realizations is shown in [Fig 9](#).

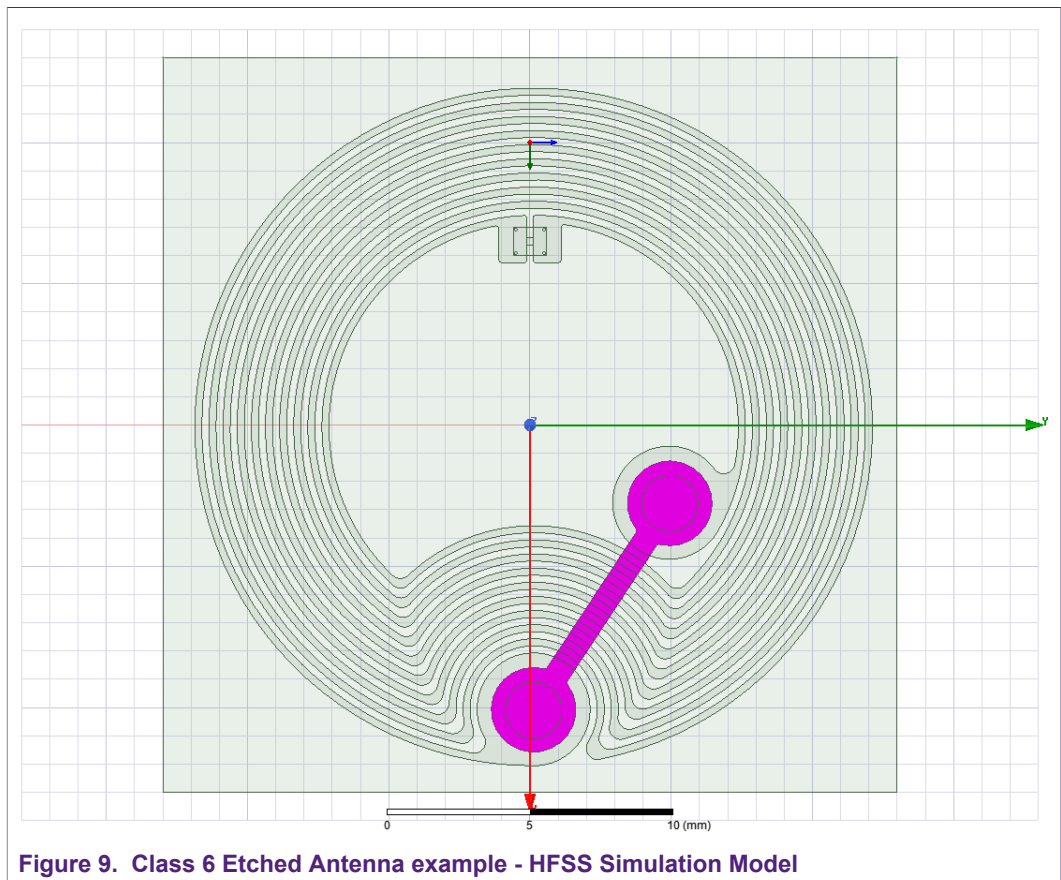

**Figure 9. Class 6 Etched Antenna example - HFSS Simulation Model**

Geometrical parameters of this antenna design is shown in [Table 5](#).

**Table 5. Geometrical Parameters of a Class 6 Etched Antenna design**

Parameter	Value
Antenna Diameter, mm	24
Material:	Aluminum
Trackwidth, mm	0,25
Gap between tracks, mm	0,25
Track thickness (coil), mm	0,03
Track thickness (bridge), mm	0,01
Number of Turns	10
Carrier Material:	Polyester

Parameter	Value
Carrier Thickness, mm	0,038
Carrier Dielectric constant, Er:	3,2

and simulative electrical parameters are presented in [Table 6](#).

**Table 6. Electrical Parameters of a Class 6 Etched Antenna design**

Parameter	Value
SRF, MHz	77,4140
R (@1MHz), Ohm	2,2765
L (@1MHz), uH	2,5668
R (@13,56MHz), Ohm	3,8604
L (@13,56MHz), uH	2,6054
C, pF	1,64
Cic, pF	50
Fres_PICC, MHz	13,9300

The drawing of this antenna (in DXF Format) is available and attached to this application note.

## 2.9 Required transponder bandwidth for (PICC --> PCD) data transfer

The demand for data transfer sets certain requirements on the transponder bandwidth  $B$ , which limits the transponder quality factor  $Q_T$ . The needed bandwidth is related to the modulation scheme, coding and data rates, used.

The highest data rate, which is defined in the standard, requires the largest transponder bandwidth.

Figure 10 demonstrates how this bandwidth can be calculated for 424 bit/s data rate.

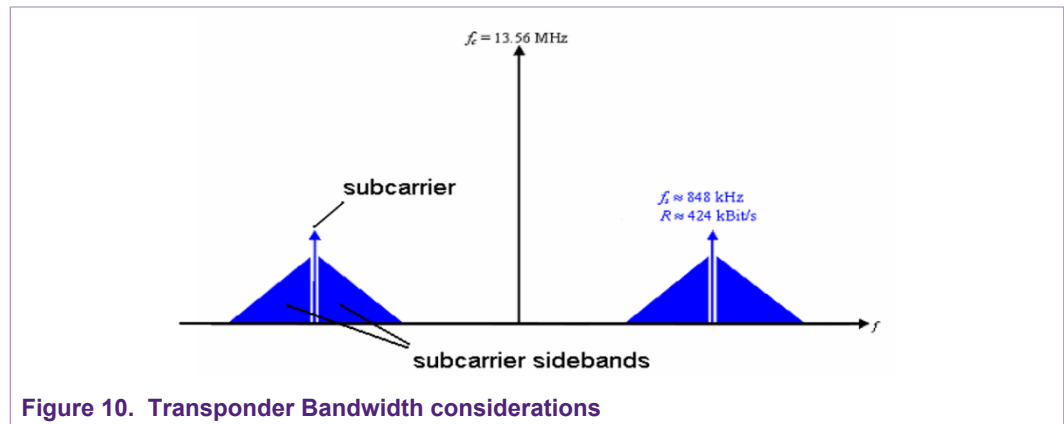


Figure 10. Transponder Bandwidth considerations

Other possible data rates and their relationship to their associated required bandwidth is given in Table 7.

Table 7. Theoretical PICC needed bandwidth for a data transfer with different data rates


Data rates [kbps]	B [MHz]
106	1,8
212	1,9
424	2,1
848	2,5
106	1,8

**Note:** if a transponder bandwidth is smaller, as recommended, this does not automatically mean that the communication will not be possible. What will happen is that the sideband levels of the card answer will be damped more than 3 dB. It is not recommended, but still sufficient for successful communication.

**Note for higher antenna classes (Class 2 to Class 6):** The inductance of the coil size reduces the coil size. It is recommended to use 50pF input capacitance IC versions for antenna sizes smaller than Class 1. This results in the increase of the transponder factor,  $Q_T$ . It is recommended to control resulting  $Q_T$  or bandwidth  $B$  of the new designed small transponder, to enable successful communication for all desired data rates.

### 3 References

---

1. AN11093 Card Coil Design Guide, Document Number: 0117\*\*<sup>1</sup> 
2. PICC and VICC Resonance Frequency Measurement
3. M. Gebhart, Air Interface, Antennas and Signals in Contactless Near-Field Communication 2nd lecture in Selected Topics of Advanced Analog Chip Design, 439.224
4. Contactless Card Standard ISO/IEC 14443-1:2018



---

<sup>1</sup> \*\* ... BU S&C document version number



## 4 Legal information

### 4.1 Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### 4.2 Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors. In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory. Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification. Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product

design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products. NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Evaluation products** — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer. In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages. Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

**Translations** — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

### 4.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

**MIFARE** — is a trademark of NXP B.V.

**DESFire** — is a trademark of NXP B.V.

**Tables**

Tab. 1.	Abbreviations .....	3	Tab. 5.	Geometrical Parameters of a Class 6 Etched Antenna design .....	13
Tab. 2.	PICC coil design recommendation .....	6	Tab. 6.	Electrical Parameters of a Class 6 Etched Antenna design .....	14
Tab. 3.	Geometrical Parameters of a Class 1 etched antenna design .....	10	Tab. 7.	Theoretical PICC needed bandwidth for a data transfer with different data rates .....	15
Tab. 4.	Electrical Parameters of a Class 1 etched antenna design .....	10			

Figures

Fig. 1.	Different Coil antenna sizes according to ISO/IEC 14443-1 .....	4	Fig. 6.	Loaded resonance frequency (14,56 MHz) and Quality factor (6,5) - Prototype .....	11
Fig. 2.	Class 1 antenna examples (with two different parameters) .....	8	Fig. 7.	Unloaded resonance frequency (15,39 MHz) and Quality factor (85,3) - Prototype .....	12
Fig. 3.	Typical parameters of different realizations of class 1 card antennas .....	9	Fig. 8.	The label sensitivity (Hmin) at 13,56 MHz - Prototype .....	12
Fig. 4.	Class 1 Etched Antenna example - HFSS Simulation Model .....	9	Fig. 9.	Class 6 Etched Antenna example - HFSS Simulation Model .....	13
Fig. 5.	Class 1 Etched Antenna example - Prototype .....	11	Fig. 10.	Transponder Bandwidth considerations .....	15

## Contents

<b>1</b>	<b>Introduction .....</b>	<b>3</b>
1.1	How to use this document .....	3
1.2	Terms and Abbreviations .....	3
<b>2</b>	<b>Card Coil Design Notes for MIFARE DESFire Light .....</b>	<b>4</b>
2.1	Different classes of antenna according to ISO/IEC 14443-1 .....	4
2.2	Average card coil area .....	4
2.3	Coil Q-Factor .....	4
2.3.1	Measurement of Coil Q-Factor .....	5
2.4	Definition for “unloaded” and “loaded” conditions. ....	5
2.5	Loaded resonance frequency of the transponder .....	5
2.5.1	Measurement of loaded resonance frequency of the transponder .....	5
2.6	NXP recommendation for PICC coil design .....	5
2.7	Practical design hints and recommendations for 17 pF chip version .....	7
2.7.1	Class 1 wire wound antennas .....	7
2.7.2	Class 1 etched antennas .....	9
2.8	Practical design hints and recommendations for 50 pF chip version .....	13
2.8.1	Class 6 etched antenna .....	13
2.9	Required transponder bandwidth for (PICC --> PCD) data transfer .....	15
<b>3</b>	<b>References .....</b>	<b>16</b>
<b>4</b>	<b>Legal information .....</b>	<b>17</b>

---

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

---

© NXP B.V. 2019.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

Date of release: 31 January 2019

Document identifier: AN12342

Document number: 522610